

## Lab 5 & 6: Assignment 1 (10 Marks)

Date for Showing the output to Instructor (No Deduction): 17/09/2021 between 11AM-1PM

Due Date for final submission through CMS: 17/09/2021 9:00 PM

Name: Vishwas Vasuki Gautam

ID No: 2019A3PS0443H

**Problem Statement:** Design a state machine to control the tail lights of a 1965 Ford Thunder bird (Figure 1). The tail lights are composed of three lights on each side which operate for the turns as shown in figure 2. The state machine has two inputs (**LEFT, RIGHT**) and 6 outputs (**LC, LB, LA, RA, RB and RC**). When (**RIGHT=0 and LEFT=0**) or when (**RIGHT=1 and LEFT=1**) no lights will turn ON. If (**RIGHT=0 and LEFT=1**) then lights LC, LB, and LA will be ON as shown in figure 2(a) indicating **LEFT** turn. If (**RIGHT=1 and LEFT=0**) then lights RA, RB, and RC will be ON as shown in figure 2(b) indicating **RIGHT** turn. In addition to LEFT and RIGHT there are two more inputs **Clk** and **Reset** for normal operation of FSM. When **Reset** is enabled all lights will be OFF. The flashing rate of LEDs is 2Hz (i.e. the time between two successive states is 0.5s).

**PIN Assignment:**

**Inputs:** RIGHT F22; LEFT G22;

**Outputs:** LC U14; LB U19; LA W22; RA U22; RB T21; RC T22;

 


Figure 1

 


Figure 2(a)


Figure 2(b)

Figure 2

(Please refer to the file named “Vivado\_Design\_Flow\_All\_Steps.pdf” for a review of all the steps in the design flow)

1. **Question:** Draw the FSM (can be an image) with proper description.

Answer:

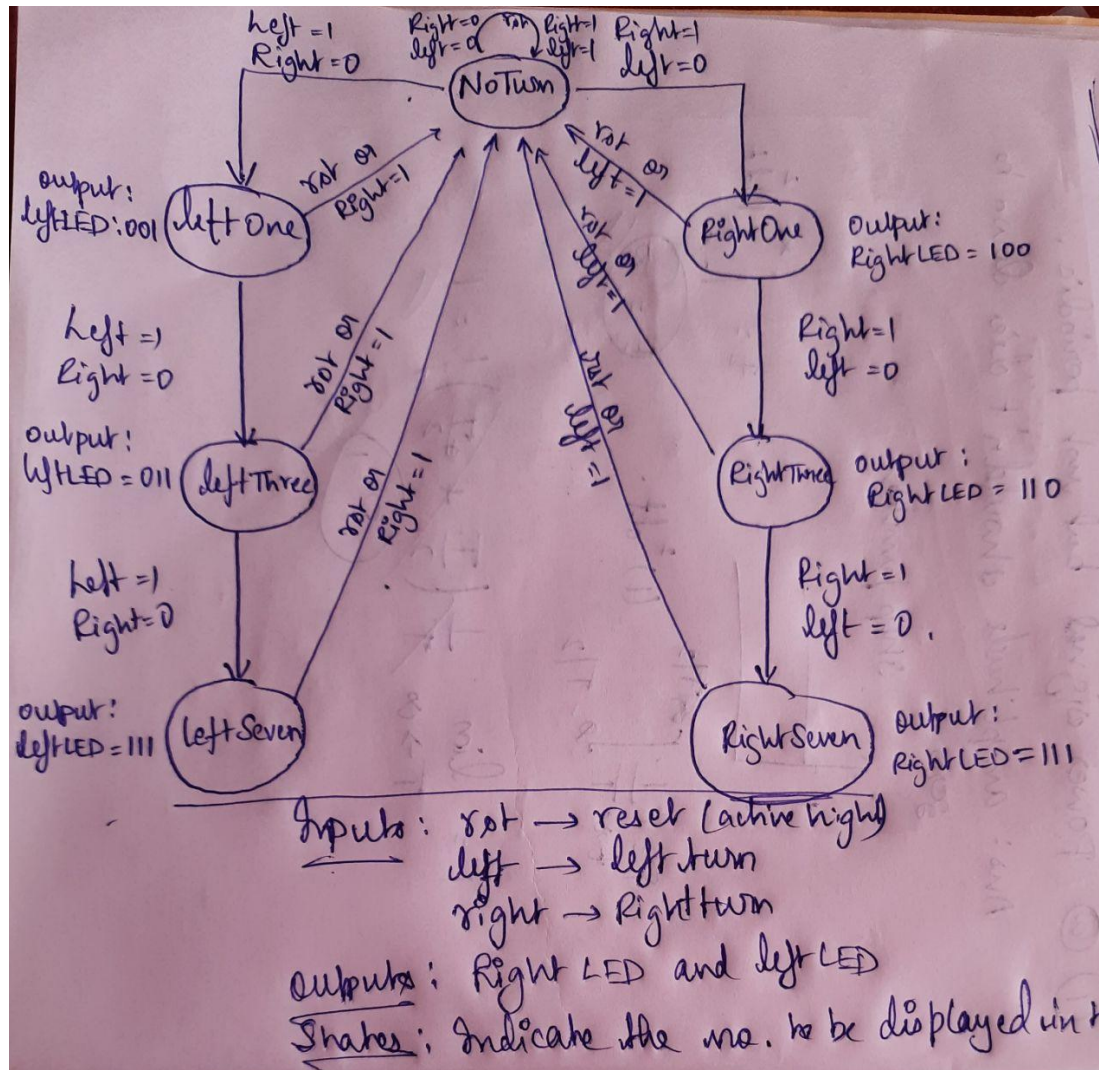

2. Create a Vivado Project and write Verilog code (**Car\_FSM.v** with comments) for implementing the above FSM.

**Question:** Paste the image of verilog code Car\_FSM.v.

Answer:

```
Car_FSM.v
F:/CompArch/FPGA_Lab/Lab5and6/project_2/project_2.srcs/sources_1/new/Car_FSM.v

// VISHWAS VASUKI GAUTAM - 2019A3PS0443H
module Car_FSM(
    input clk,
    input rst,
    input right,
    input left,
    output reg [2:0] rightLED,
    output reg [2:0] leftLED
);

    reg [25:0] clkDiv;

    parameter noTurn = 3'b000;
    parameter leftOne = 3'b001, leftThree = 3'b010, leftSeven = 3'b011; // Indicates the states for left turn
    parameter rightOne = 3'b100, rightThree = 3'b101, rightSeven = 3'b110; // Indicates the states for right turn

    reg [2:0] presentState, nextState;

    initial begin
        clkDiv <= 0;
    end

    always @(posedge clk) // Clock division
    begin
        clkDiv <= clkDiv + 1;
    end

    always @(posedge clkDiv[25], posedge rst) // State register for initialisation
    begin
        if(rst)
            presentState <= noTurn;
        else
            presentState <= nextState;
    end
end
```

```
Car_FSM.v
F:/CompArch/FPGA_Lab/Lab5and6/project_2/project_2.srcs/sources_1/new/Car_FSM.v

// Calculating the next state based on the inputs and the present state
always @(presentState, right, left)
begin
    case(presentState)
        noTurn:
            if(left ^ right == 0)
                nextState <= noTurn;
            else if(left == ~right)
                nextState <= leftOne;
            else if(~left == right)
                nextState <= rightOne;

        leftOne:
            nextState <= (left == ~right)? leftThree: noTurn;

        leftThree:
            nextState <= (left == ~right)? leftSeven: noTurn;

        leftSeven:
            nextState <= noTurn;

        rightOne:
            nextState <= (~left == right)? rightThree: noTurn;

        rightThree:
            nextState <= (~left == right)? rightSeven: noTurn;

        rightSeven:
            nextState <= noTurn;

    endcase
end
```

```

always @(presentState)//Calculating the output based on the present state
begin
    case(presentState)
        noTurn: begin
            rightLED <= 3'b000;
            leftLED <= 3'b000;
        end
        leftOne: begin
            rightLED <= 3'b000;
            leftLED <= 3'b001;
        end
        leftThree: begin
            rightLED <= 3'b000;
            leftLED <= 3'b011;
        end
        leftSeven: begin
            rightLED <= 3'b000;
            leftLED <= 3'b111;
        end
        rightOne: begin
            rightLED <= 3'b100;
            leftLED <= 3'b000;
        end
        rightThree: begin
            rightLED <= 3'b110;
            leftLED <= 3'b000;
        end
        rightSeven: begin
            rightLED <= 3'b111;
            leftLED <= 3'b000;
        end
    endcase
end
endmodule

```

3. Write the test bench **Test\_Car\_FSM.v** and simulate your design to check the functionality.

**Question:** Paste the image of test bench verilog code **Test\_Car\_FSM.v**

Answer:

```


Car_FSM_test.v
F:/CompArch/FPGA_Lab/Lab5and6/project_2/srcs/sim_1/new/Car_FSM_test.v

23 module Car_FSM_test(
24
25 );
26     reg clk, rst, right, left;
27     wire [2:0] rightLED, leftLED;
28     // module instantiation
29     Car_FSM car(.clk(clk), .rst(rst), .right(right), .left(left), .leftLED(leftLED), .rightLED(rightLED));
30
31     always #5 clk = ~clk;
32
33     initial // Checking all the possible inputs
34     begin
35         clk <= 0;
36         rst <= 1;
37         right <= 0;
38         left <= 0;
39         #5 rst <= 0;
40         #5 right <= 1;
41         #30 right <= 0;
42         #60 left <= 1;
43         #30 left <= 0;
44         #60 left <= 1;
45         #5 right <= 1;
46
47         #100 $finish;
48     end

```

**Question:** Paste the image showing the simulated waveforms for FSM (Behavioral Simulation). Clearly show the LEFT turn and RIGHT turn Cases.

Answer:

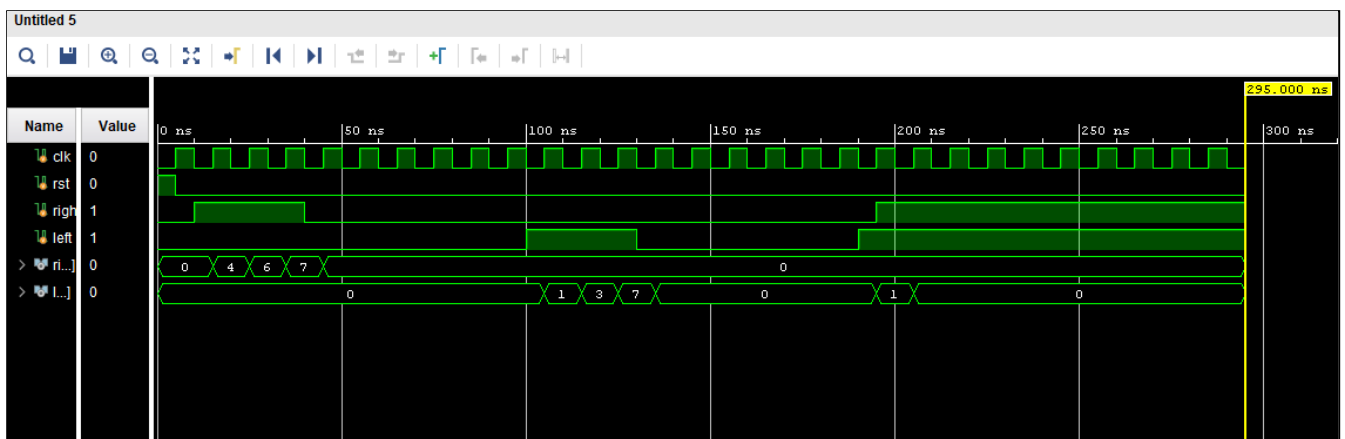


4. Add clock division code to **Car\_FSM.v** such that the actual input **Clk (Y9 pin with frequency of 100MHz)** is converted to Clock of frequency 2Hz. This 2Hz signal is used as clock for running the FSM.
5. Plan your I/O mapping (using **I/O planning** option) such that actual input **Clk** is connected to internal clock pin **Y9**, **Reset** is connected to push button switch, other inputs (**LEFT** and

**RIGHT)** are connected to DIP switches and outputs are connected to LEDs. In the ZedBoard, the pin numbers indicating the DIP switches, LEDs and internal clock are listed in table uploaded in CMS. Save the mapping information as **Car\_FSM.xdc**.

6. Synthesize (**Run Synthesis**).


**Question:** Paste the image showing the schematic after synthesis.

Answer:

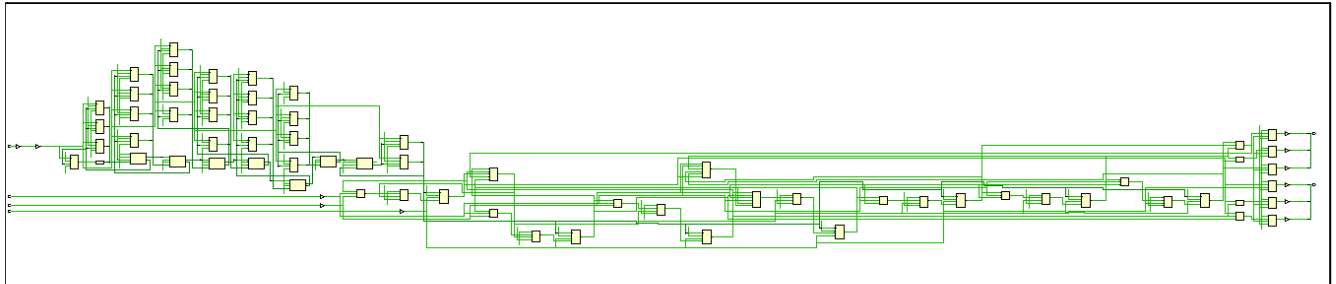

**Question:** Check the summary report and report hardware utilization for the FSM implementation.

Answer: Hardware utilization

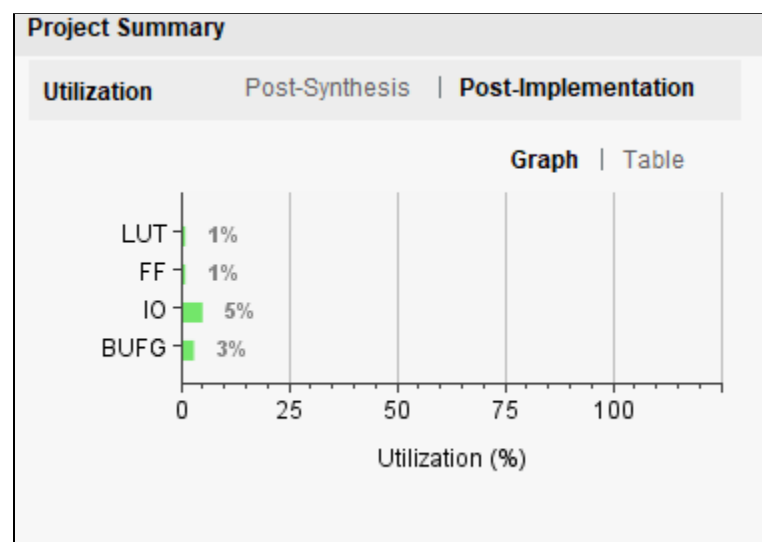

Utilization		Post-Synthesis   Post-Implementation	
		Graph   Table	
Resource	Utilization	Available	Utilization %
LUT	14	53200	0.03
FF	33	106400	0.03
IO	10	200	5.00
BUFG	1	32	3.13

7. Implement the design (**Run Implementation**).
8. **Generate Bitstream** and port your design on to FPGA (**Open Hardware Manager** **New Target** ... **Program Device**)
9. **Check the output on FPGA.**
10. **Show the output to the instructor.**
11. **Submit following files as a Zipped folder with file name as <Student1\_ID\_No>\_<Name>.zip through CMS before due date.**
  - 1) **Completed Document**
  - 2) **Car\_FSM.v (with proper comments)**
  - 3) **Test\_Car\_FSM.v (with proper comments)**
  - 4) **Car\_FSM.xdc.**
  - 5) **Car\_FSM.bit**